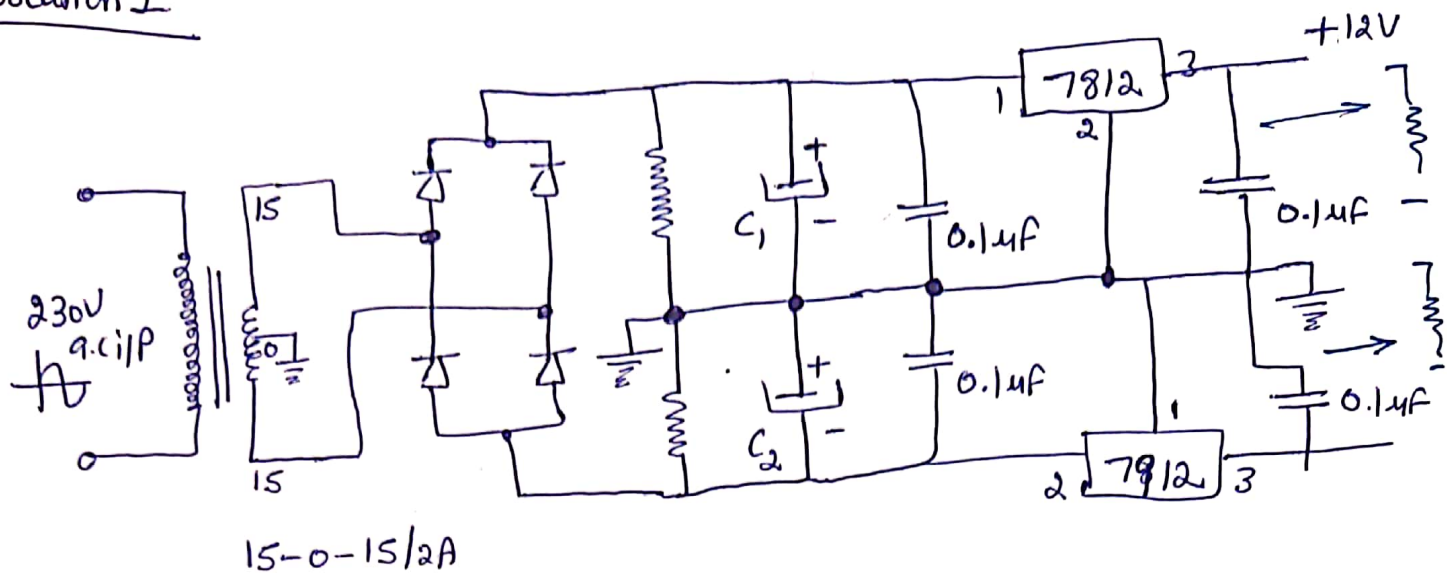


Solution 2



Given $V_r = 0.5V$

$$V_r = \frac{1}{2} \cdot \frac{V_p}{R C f_m}$$

$$0.5 = \frac{1}{2} \cdot \frac{15\sqrt{2}}{(1000)(C)50}$$

$$C = \frac{21.21}{5,0000}$$

$$C = 4.242 \times 10^{-4} \times \frac{100}{100}$$

$$C = 424.2 \mu F \quad \checkmark$$


$C_1 = C_2 = 330 \mu F$ and $100 \mu F$ Connected in parallel

Diode 1N4007 \rightarrow ~~Current~~ It can pass current upto 1A.
and PIV rating 1000 Volts.

$$\text{Secondary Voltage} = 15\sqrt{2} = 21V$$

So voltage rating of Capacitor should be more than 21V

Solution: 2

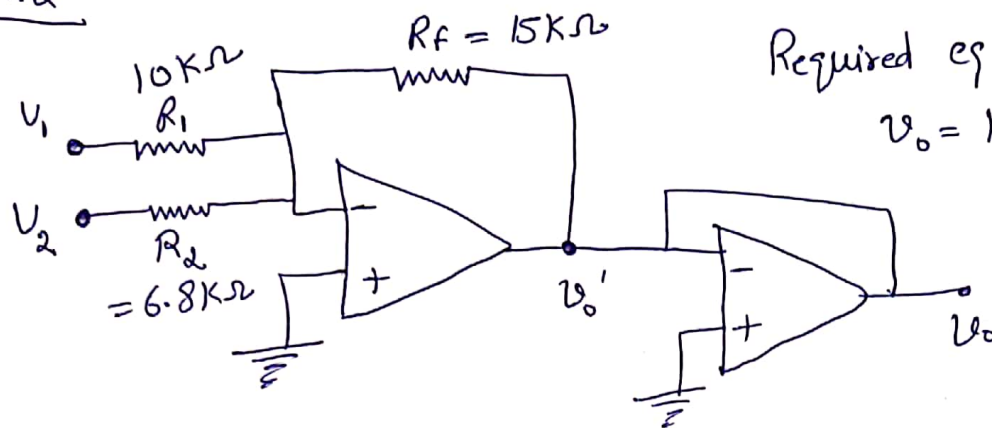

$$V_o' = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right]$$

$$\frac{R_F}{R_1} = 1.5 \quad ; \quad \frac{R_F}{R_2} = 2.2$$


$$\frac{15K\Omega}{10K\Omega} = 1.5 \quad ; \quad \frac{15K\Omega}{6.8K\Omega} = 2.2$$

$$V_o = -V_o'$$

$$\therefore V_o = + \left[1.5V_1 + 2.2V_2 \right]$$

Q.3

Solution:

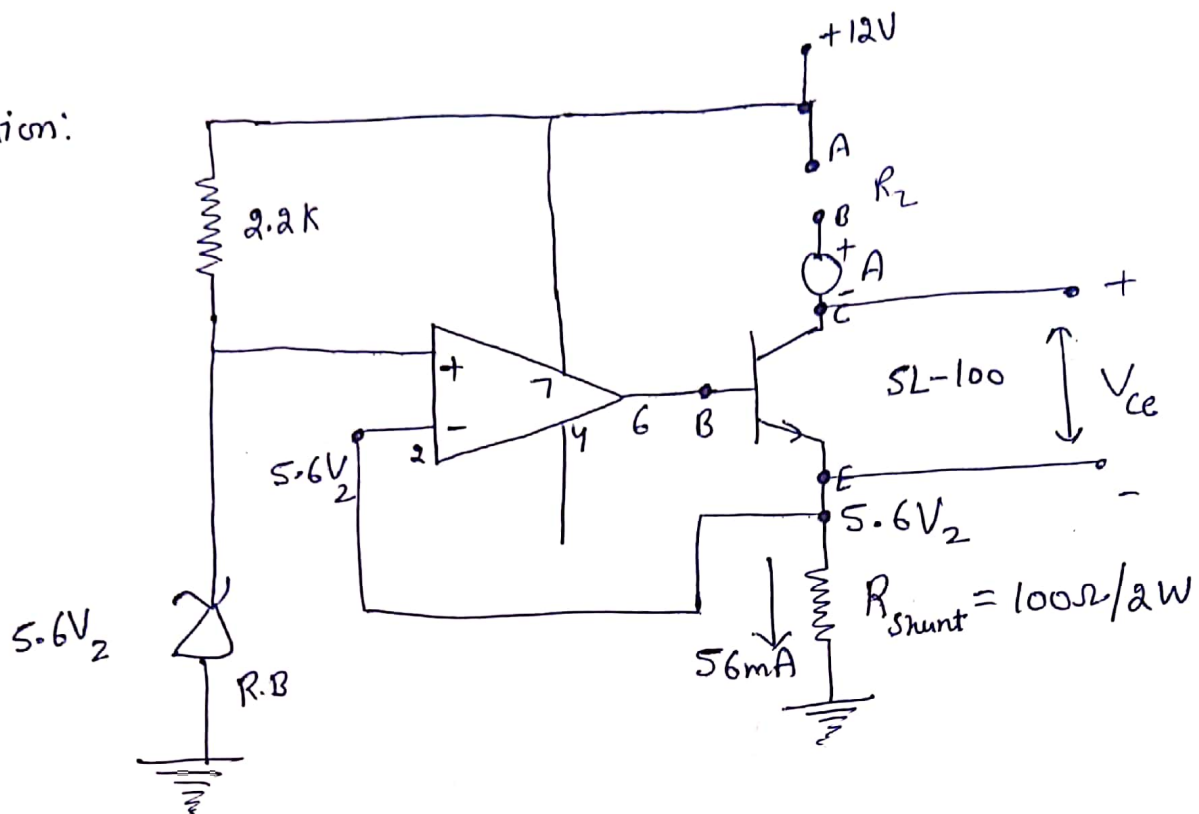

For $V_2 = 5.6V_2$

R_L	V_{ce} drop across transistor	Load current (I_L)
① $R_L = 0$	$V_{ce} = V_{cc} - V_{shunt}$ $= 12 - 5.6$ $V_{ce} = 6.4V$	56mA
② $R_L = 10\Omega$	$V_{ce} = V_{cc} - V_{shunt} - I_L R_L$ $= 12 - 5.6 - \frac{56}{1000} \times 10$ $= 12 - 5.6 - 0.56$ $= 5.84V$	56mA
③ $R_L = 47\Omega$	$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 47$ $= 12 - 5.6 - 2.632$ $= 3.768V$	56mA
④ $R_L = 68\Omega$	$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 68$ $= 12 - 5.6 - 3.808$ $= 2.592V$	56mA
⑤ $R_L = 82\Omega$	$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 82$ $= 12 - 5.6 - 4.592$ $= 1.808V$	56mA

$$\textcircled{5} R_L = 100\Omega$$

$$V_{ce} = 12 - 5.6 - \frac{5.6}{1000} \times 1000$$

$$56\text{mA}$$

$$= 12 - 5.6 - 5.6$$

$$V_{ce} = 0.8\text{V}$$

$$\textcircled{6} R_L = 150\Omega$$

$$V_{ce} = 12 - 5.6 - \frac{5.6}{1000} \times 1500$$

$$= 12 - 5.6 - 8.4$$

$$V_{ce} = -2\text{V}$$

So, this ~~constant~~ circuit will provide constant current of 56mA upto $R_L = 100\Omega$. After, this, for higher values of load resistor, base current has no control over collector current as transistor is in saturation now. Here load resistor controls load current no.