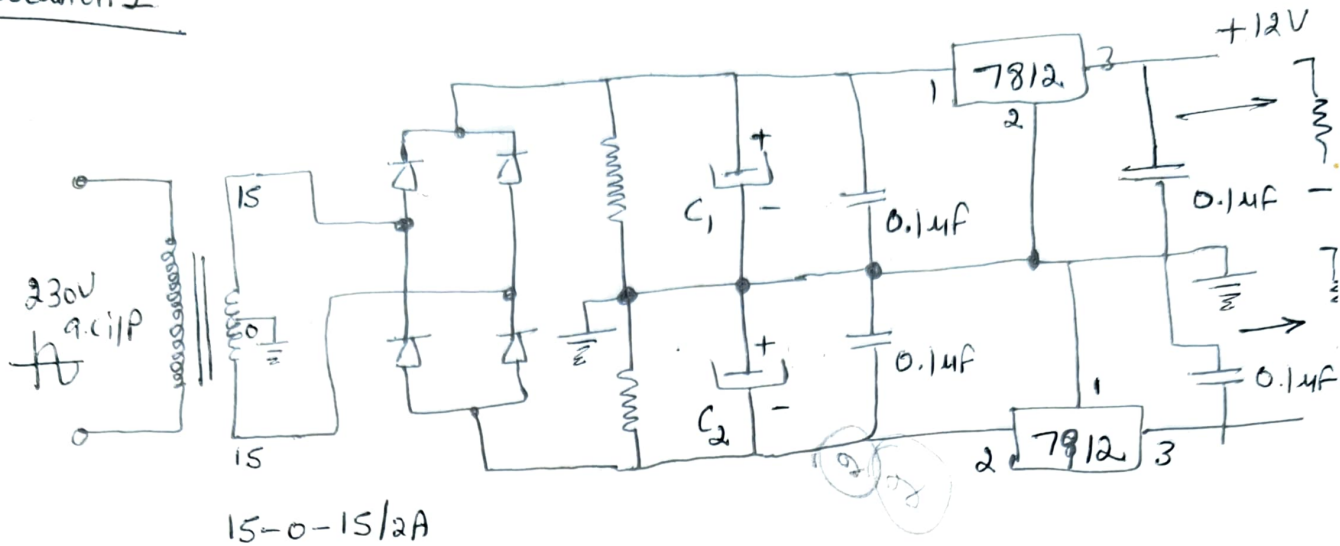


## Solution 2



Given  $V_Z = 0.5V$

$$V_Z = \frac{1}{2} \cdot \frac{V_P}{R C f_n}$$

$$0.5 = \frac{1}{2} \cdot \frac{15\sqrt{2}}{(1000)(C)50}$$

$$C = \frac{26.21}{5,0000}$$


$$C = 4.242 \times 10^{-4} \times \frac{100}{100}$$

$$C = 424.2 \mu F$$

$C_1 = C_2 = 330 \mu F$  and  $100 \mu F$  Connected in parallel

Diode 1N4007 → ~~Current~~ It can pass current upto 1A.  
and PIV rating 1000 Volt.

Solution: 2

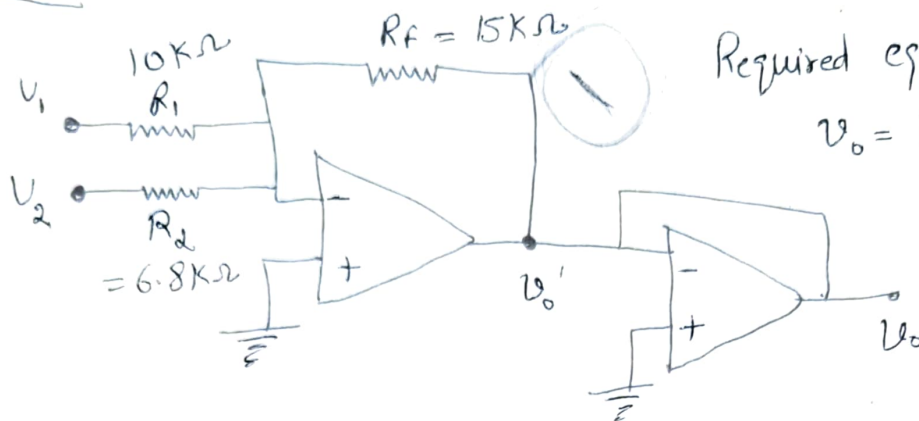

$$V_0' = - \left[ \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right]$$


$$\frac{R_F}{R_1} = 1.5 \quad ; \quad \frac{R_F}{R_2} = 2.2$$

$$\frac{15K\Omega}{10K\Omega} = 1.5 \quad ; \quad \frac{15K\Omega}{6.8K\Omega} = 2.2$$

$$V_0 = - V_0'$$

$$\therefore V_0 = + [1.5V_1 + 2.2V_2]$$

Solution:

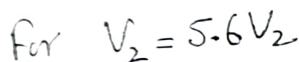

$R_L$	$V_{ce}$ drop across transistor	Load current ( $I_L$ )
① $R_L = 0$	$V_{ce} = V_{cc} - V_{shunt}$ $= 12 - 5.6$ $V_{ce} = 6.4V$	56mA
② $R_L = 10\Omega$	$V_{ce} = V_{cc} - V_{shunt} - I_L R_L$ $= 12 - 5.6 - \frac{56}{1000} \times 10$ $= 12 - 5.6 - 0.56$ $= 5.84V$	56mA
③ $R_L = 47\Omega$	$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 47$ $= 12 - 5.6 - 2.632$ $= 3.768V$	56mA
④ $R_L = 68\Omega$	$V_{ce} = 12 - 5.6 - \frac{56 \times 68}{1000}$ $= 12 - 5.6 - 3.808$ $= 2.592V$	56mA
⑤ $R_L = 33\Omega$	$V_{ce} = 12 - 5.6 - \frac{56 \times 33}{1000}$ $= 12 - 5.6 - 1.848$ $= 4.552V$	56mA

$$\textcircled{5} R_L = 100\Omega$$

$$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 1000$$

$$= 12 - 5.6 - 5.6$$

$$V_{ce} = 0.8V$$

56mA

$$\textcircled{6} R_L = 150\Omega$$

$$V_{ce} = 12 - 5.6 - \frac{56}{1000} \times 150$$

$$= 12 - 5.6 - 8.4$$

$$V_{ce} = -2V$$

So, this ~~constant~~ circuit will provide constant current of 56mA upto  $R_L = 100\Omega$ . After, this, for higher values of Load Resistor, Base current has no control over collector current as transistor is in saturation now. Here Load Resistor controls Load Current No.